# **Developer Guide iOS Power Supply**

#### • System Overview

The iOS Power Supply is a functional bench power supply designed for electrical engineering students. We require smooth power output with minimal output ripple to power and test our creations. The design must be compact, robust and accept US standard plugs for 120 V mains and our USB devices. Since we are so connected to our smart phones, this power supply will feature Bluetooth connectivity through an iOS application for convenient control of both outputs. As an added feature we have included a touch screen that can also control both channels and two dedicated USB charge ports.


## • Electrical Specifications

Two electrically isolated outputs with 0 to 24V @ 3A output. 120V input with 2A overcurrent protection. The main outputs have resolution of 10mV voltage increments and 50mA current increments. Two 5V USB dedicated charge port controllers that can supply up to 2100mA to high power external devices.

#### • User Guide


The system does not require any setup by the user other than the installation of the iOS application onto their device. The main outputs can be driven by the onboard touchscreen or through the application by incrementing or decrementing the desired voltage or current parameters with buttons. The actual output is visible from the application viewing window and the touchscreen.

## • Design Artifact Figures

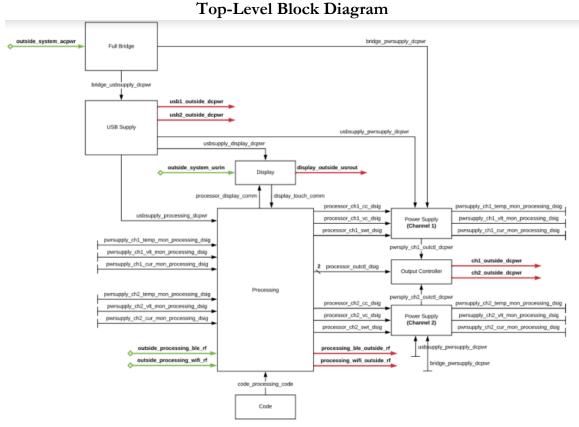


The top-level block diagram shows a general overview of how the smaller blocks are interconnected to form the main power, USB power, and control paths. Internal signals are thin black lines, outputs from the system are in red, and the input signals from the outside are colored in green. The main power path begins at the full bridge block, which supplies 32VDC to the USB and POWER Supply blocks. The USB Supply block is also in control of the 5V to the Processing microcontroller, 5V and -5V rail needed to control the additional control circuitry that drive the Power Supply block. The signal, code\_processing\_code, is a pseudo signal that commands the pi and its functionality.

## **Power Supply Schematic**

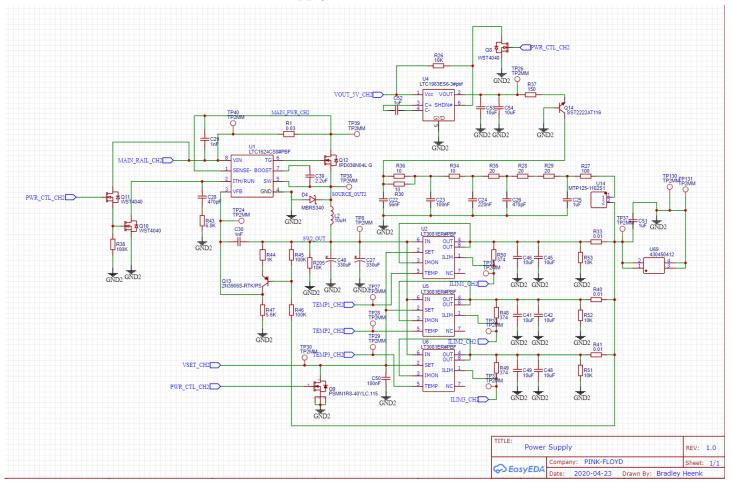


There are two Power supply circuits. They contain all of the elements required to drive the main output terminals to their voltage and current setpoints. There are adequate test pins strategically located to allow for thorough circuit debugging. The LT3081 integrated circuits are the linear voltage regulators wired in parallel such that their output currents sum together. Each is able to supply 1.5 amps max. The LTC1624 is the switching regulator that steps down the 32VDC supply to 1.6 volts above the linear output. This is to increase the efficiency and power consumption of the linear voltage regulators. LTC1983 is a current sinc that will allow the output to be pulled to 0 volts. This was required because the LTC3081s have a minimum output of 1.5 volts. The MOSFETs driven by PWR\_CTRL\_CH2 function as off switches for the circuit.

#### **Current Control Schematic**

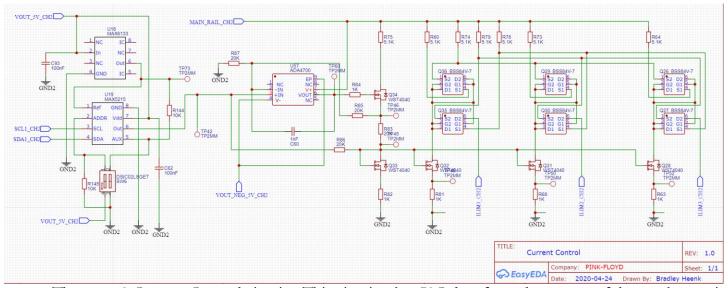


There are 2 Current Control circuits. This circuit takes I2C data from the output of the raspberry pi at SCL1\_CH2 and SDA1\_CH2 convert it to an analog signal with the MAX5215 14-bit DAC to control the output current. The signal is electrically isolated from the main power circuit through an ADA4700. The CMOS circuit is a current mirror that drives constant current to the ILIMx\_CH2 pins at the linear regulators in the Power Supply circuit.

#### **Voltage Control Schematic**

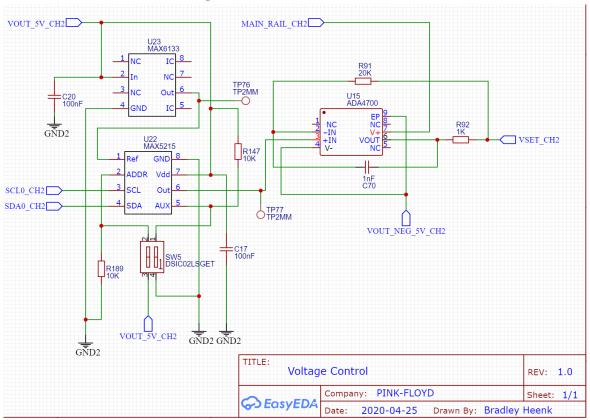


There are 2 voltage control circuits. This one takes in I2C data from the pi on SCL0\_CH2 and SDA0\_CH2 converts it to an analog signal with the MAX5217 16-bit DAC. The analog signal is fed through the ADA4700 to drive the voltage set pin VOUT\_NEG\_5V\_CH2 and VSET\_CH2 that connect to the linear regulators in the Power Supply circuit.

# **Temperature Control Schematic**

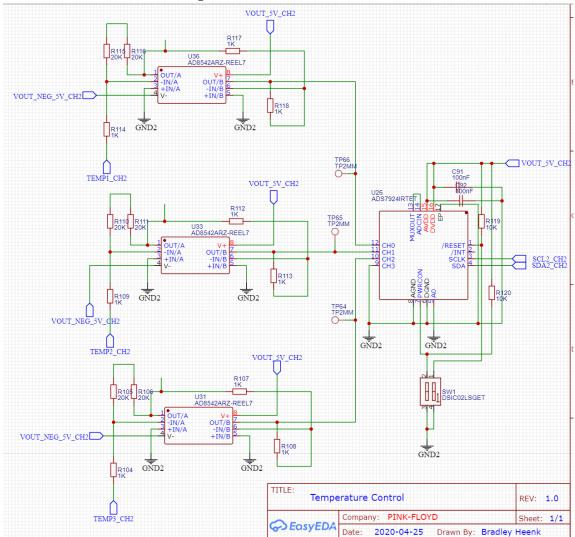


There are two Temperature Control circuits that take in temperature readings from the linear regulators as an analog signal from TEMPx\_CH2. The signal is converted to a digital signal with the ADS7924 and fed to the pi through SDA2\_CH2 and SCL2\_CH2 signals via I2C communication protocol. These temperature readings are used by the pi to regulate a PWM controlled fan if the temperature exceeds some maximum threshold.

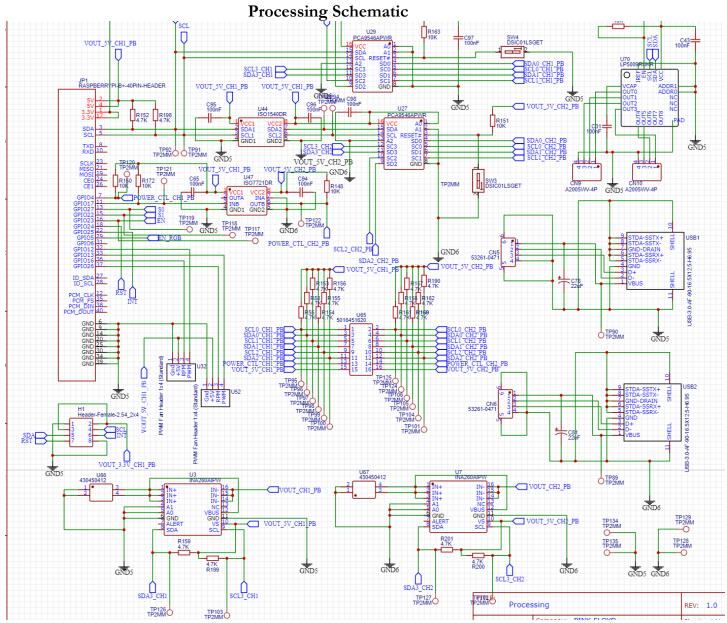


The processing circuit interfaces to the pi through a 40-pin connector on the left. The main function of this circuit is to feed all of the data into and out of the microcontroller. This circuit separates all of the I2C data bus lines Through PCA9546 addressing ICs. The main SDA and SCL lines from the pi are isolated through ISO1540 optocouplers. Also included in this schematic are INA260 ICs that monitor the output current with a sampling rate of 400kHz and output I2C data to be read by the pi. The output connectors for the USB dedicated charge port controllers are also featured in this schematic for the purpose of laying out the PCB's.

#### **USB Supply Schematic**

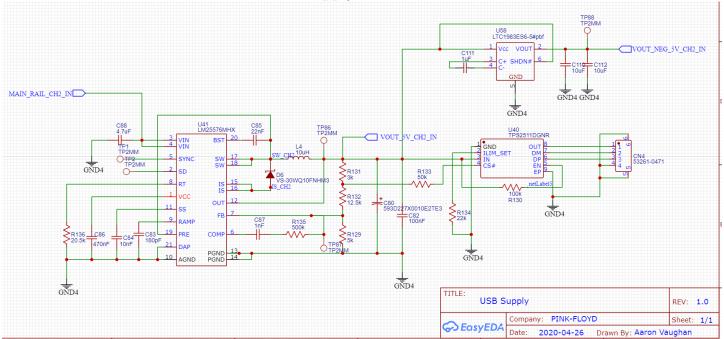

There are three USB Supply circuits in our design. One is dedicated to drive all the microcontroller power needs, and the TFT touch screen. There is one for each channel used for DCP function to drive high current devices such as iPads and tablets. The LM25576 is a switching regulator in a buck topology. It will drive 3A in this configuration at 5 to 5.1 volts. The TPS2511 is the DCP controller IC that monitors the downstream device demand for current. If the device requires more than 500 mA there is an internal MOSFET that drives the switching regulator to a slightly higher voltage through the CS pin's interaction with the feedback voltage divider circuit shown at R131. This circuit also contains an LTC1983 -5V charge pump circuit that delivers -5V to the voltage control circuit among others.

# Full Bridge Schematic

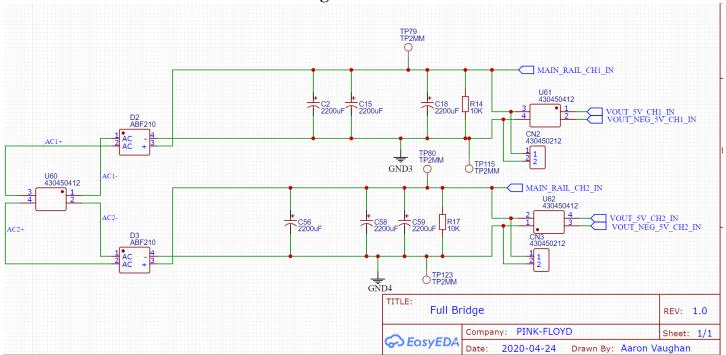

There is only one Full Bridge Circuit in our design. The ABF210 ICs are simply bridge rectifiers. The transformer supplies 26VAC to their input and after rectification the circuit provides 32VDC to the USB and Power Supply modules. This signal is passed through a low pass filter bank of capacitors and resistors to smooth the output ripple.


#### 3-D printed Enclosure

The enclosure is constructed of 5 individually printed components. The Outer shell houses the TFT display at the top opening, while the guts of the device will slide in through the end. They are held in place wit the help of the two endcaps. The endcaps have air holes of 1mm for cooling. Their size was limited to 1mm to decrease the risk of safety hazards involved with users coming in contact with the high current circuitry within. The inner components will slide in on a tray comprised of a two-piece clam shell configuration. The toroidal transformer mounts to the bottom with two of the PCBs and the top portion holds the processing PCB that interfaces with the pi as well as the raspberry pi itself. Please see the images below for greater detail.






The Inner Clam Shells

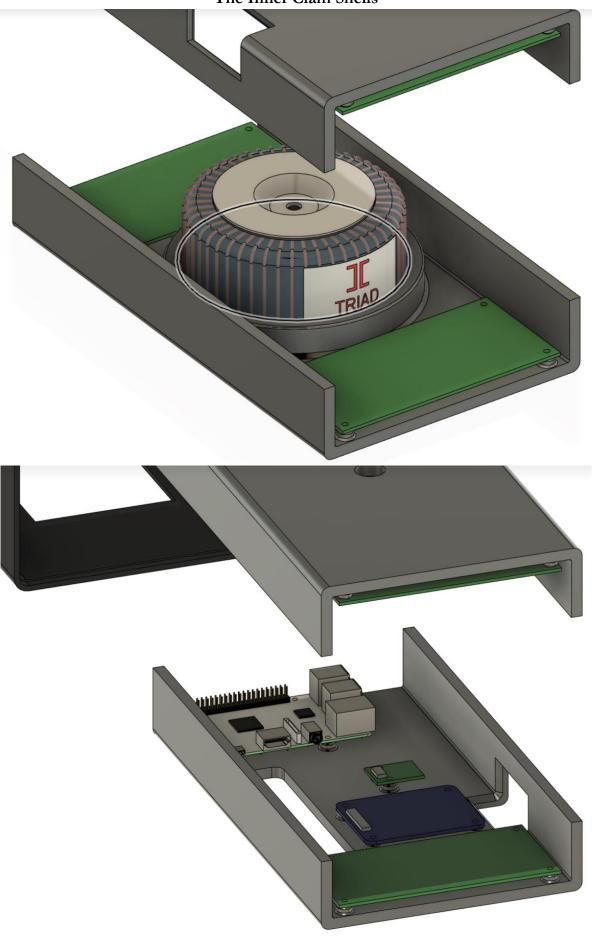


The End Caps

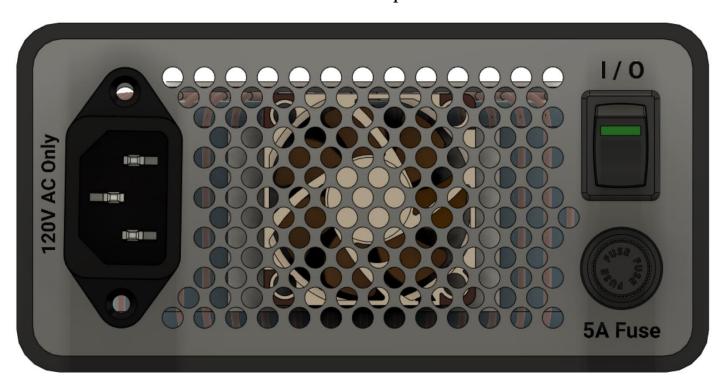


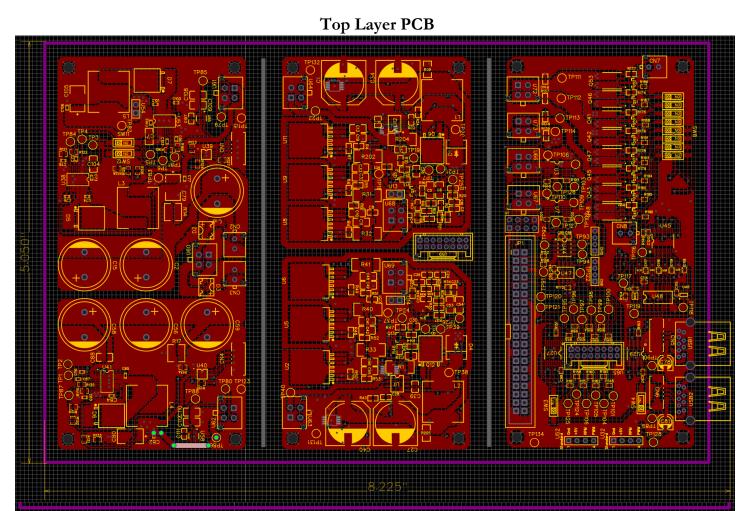
#### PCB Information


The PCB is roughly 8 1/4 inches by 5 inches in total. The entire PCB was designed to be separated into three smaller sections delineated by the thick grey lines which are actually channels milled out of the PCB material for easy separation. The first section (left) contains the full bridge rectification, and all three of the 32V to 5V DC-DC Buck regulator circuits along with their -5V charge pump circuits. The seconds section (middle) is the high current switching regulators and linear regulators that make up the two main output channels. The third section (right) is the control circuit which interfaces all of the devices that communicate to the raspberry pi. This section is sensitive to noise and needed to be completely isolated from the noisy switching supplies.



Layer 2 (inner) PCB


This layer is the power ground for all sections.

Layer 3 (inner) PCB

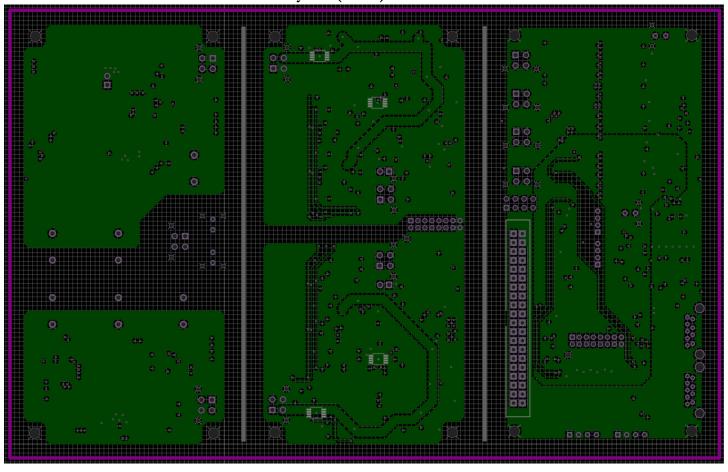

This layer is the analog ground for all sections.

Layer 4 (bottom) PCB

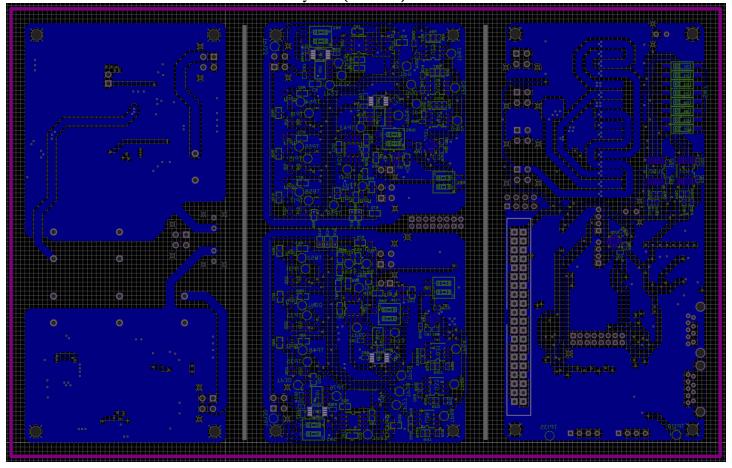

The bottom traces are surrounded by the analog ground planes to further isolate their signals from noise.

3-D Top View



3-D Bottom View



# • Part Information

D	Name	Quantity	Manufacturer Part	Manufacturer	Supplier	Supplier Part
1	N-channel MOSFET	24	WST4040	Winsok Semicon	LCSC	C377863
2	150	2	AR03DTCX1500	Viking Tech	LCSC	C319857
3	100nF	2	CL10F104ZB8NNNC	SAMSUNG	LCSC	C1688
4	22uF	2	UZG0J220MCL1GB	Nichicon	LCSC	C250865
5	2mm Test Pin		N/A	N/A	N/A	N/A
	0.01		RLM25FEER010		LCSC	C192580
	1K		ARG03FTC1001	Viking Tech	LCSC	C217840
	20K		AR02DTD2002	_	LCSC	C319759
	220uF		593D227X0010E2TE3	VISHAY	Digi-Key	478-6163-1-ND
	10K		AR06DTDV1002		LCSC	C319943
11	1K		AR03BTDX1001		LCSC	C319812
12	Linear regulator	2	LTC1624CS8#PBF		LCSC	C107744
13	470pF	2	CL10B471KB8NNNC	SAMSUNG	LCSC	C22396
14	Header-Female-2.54_2x4	1	220S-2*4P H=8.5MM Ytype Gold-plated	Ckmtw	LCSC	C124422
15	2200uF	6	2200uF 50V ±20%	ValuePro	LCSC	C13917
16	1K	2	AR03BTCX1001A010	Viking Tech	LCSC	C374414
17	10	6	AR03DTCX0100	Viking Tech	LCSC	C319921
	DPST dip switch		DSIC02LSGET	KE	LCSC	C54949
	OR gates		SN74LVC1G32DCKR	TI	LCSC	C7840
	_			Texas Instruments		C366164
	Digital Isolator		ISO7721DR			
	5V reference voltage		MAX6133	Maxim Integrated	•	MAX6133BASA25+-ND
22	4.7K		AR02BTC4701	Viking Tech	LCSC	C317921
23	N-channel mosfet array	8	BUK7K6R2-40EX	Nexperia	LCSC	C458245
24	USB charge port controller	2	TPS2511DGNR	TI	LCSC	C68648
25	100nF	32	CL05B104KB54PNC	Samsung Electro-	LCSC	C307331
26	Molex connector	4	53261-0471	MOLEX	LCSC	C240847
27	6.8K	2	R0603RXX682XF10LTS	Shenzhen Eyang	LCSC	C267593
28	10K	8	RMS06JT103		LCSC	C209220
	SPST dip switch		DSIC01LSGET		LCSC	C54948
	20		AR03DTDX0200		LCSC	C319746
					LCSC	
	-5V charge pump		LTC1983ES6-5#pbf			C117346
	-3V charge pump		LTC1983ES6-5#pbf		LCSC	C117346
	56nF		CL10B563KB8NNNC	Samsung Electro-		C318655
	Molex connector 1nF	2	5016451620 CL10B102KC8NNNC		LCSC LCSC	C293576 C153291
	10K		AR02DTD1002		LCSC	C319933
	100nF		0603F104Z500CT	Guangdong TOPA		C180398
	P-channel Mosfet array		BSS84V-7	Diodes Incorporat		C459524
	4.7uF	3	CC1206ZRY5V6BB475	Yago	Digi-Key	311-2008-1-ND
	1nF		CC0603KRX7R9BB102	Yago	Digi-Key	311-1080-1-ND
	470nF		CC0603KRX5R8BB474	Yago	Digi-Key Digi-Key	311-3365-1-ND
	180pF 100nF		C0603C181J5GACTU C0603C104Z3VACTU	Yago Kmet	Digi-Key Digi-Key	399-1064-1-ND 399-1100-1-ND
	10nF		C0603C103M5RACTU	Kmet	Digi-Key	399-7842-1-ND
	22nF		C0603C223K1RACTU	Kmet	Digi-Key	399-3476-1-ND
	2.2uF	2	UMK212ABJ225KG-T	Taiyo Yuden	LCSC	C337444
	1K		AR02DTC1001	Viking Tech	LCSC	C319808
	Schottky diode		ABF210	Jingdao	LCSC	C169534
	330uF		VZH331M1HTR-1313	LELON	LCSC	C164077
	20K NPN Transistor		AR03BTDX2002 SST2222AT116	Viking Tech ROHM	LCSC LCSC	C319765 C79976
	10K		CR1218J10KE04	Ever Ohms Tech		C175611
	4-channel digital isolator		ISO7140CCDBQR	Texas Instruments		C205953
	I2C digital isolator		ISO1540DR	TI	LCSC	C179739
55	10uF		C3216X7R1V106MT000E	TDK	LCSC	C361179
	1uF		CL10A105KB8NNNC	SAMSUNG	LCSC	C15849
	1nF		GCJ216R72A102KA01D	Murata Electronics		C354376
	N-channel MOSFET		IPD036N04L G	Infineon Technolog		C152354
	100		AR03BTCX1000 MCT06030C3001EB500	Viking Tech	LCSC Digi Koy	C319953
	3k 100k		MCT06030C3001FP500 MCT06030C1003FP500	VISHAY	Digi-Key Digi-Key	MCT0603-3.00K-CFCT-NI MCT0603-100K-CFCT-NE
91	12.5k		CRCW060312K4FKEA	VISHAY	Digi-Key Digi-Key	541-12.4KHCT-ND

ID Name	Quantity	Manufacturer Part	Manufacturer	Supplier	Supplier Part
61 100k	2	MCT06030C1003FP500	VISHAY	Digi-Key	MCT0603-100K-CFCT-ND
62 12.5k	2	CRCW060312K4FKEA	VISHAY	Digi-Key	541-12.4KHCT-ND
63 50k	2	MCT06030C4992FP500	VISHAY	Digi-Key	749-1660-1-ND
64 22k	2	MCT06030C2202FP500	VISHAY	Digi-Key	MCT0603-22.0K-CFDKR-ND
65 20.5k	3	CRCW060320K5FKEA		Digi-Key	541-20.5KHCT-ND
66 500k	3	MCT06030C4993FP500	VISHAY	Digi-Key	749-1661-1-ND
67 5k	2	MCT06030C4991FP500	VISHAY	Digi-Key	MCT0603-4.99K-CFCT-ND
68 BUCK regulator	3	LM25576MHX	TI	LCSC	C14654
69 RGB LED driver	1	LP5009RUKR	Texas Instruments	Texas Instruments	Texas Instruments
70 8PST dip switch	2	DSIC08LSGET	KE	LCSC	C54953
71 374	6	ARG03FTC3740	Viking Tech	LCSC	C217990
72 USB jack	2	USB-3.0-AF-90-16.5X12.5-H6.95	LCSC	LCSC	C69073
73 N-Channel MOSFET	2	PSMN1R8-40YLC,115	Nexperia	LCSC	C88071
74 Logic Buffer	1	SN74LVC541APWR		LCSC	C113281
75 I2C Addresser	2	PCA9546APWR	Texas Instruments	LCSC	C400705
76 14-bit DAC	4	MAX5215	Maxim Integrated	Digi-Key	MAX5217BGUA+-ND
77 Shottky Diode	3	VS-30WQ10FNHM3		LCSC	C145461
78 OPAMP	6	AD8542ARZ-REEL7	ADI	LCSC	C45344
79 12-bit ADC	2	ADS7924IRTET	Texas Instruments		C201603
80 Digital resistor	6	LT3081ER#PBF	LINEAR	LCSC	C117395
81 Inverter gate	4	SN74LVC2G04DCKR	TI	LCSC	C105251
82 470pF		GRM188R72E471KW07D	Murata Electronics		C117800
83 100K	12	ARG03FTC1003		LCSC	C217682
84 1uF		CL10A105KA8NNNC		LCSC	C5673
85 100K		AR03BTC1003A010		LCSC	C374388
86 Connector		A2005WV-4P	Changjiang Conne		C225256
87 Connector		RASPBERRYPI-B+-40PIN-HEADER		adafruit	
88 Schottky diode		MBRS340		LCSC	C117937
89 Molex connector	11			LCSC	C277721
90 0.03	2	RLP25FEER030		LCSC	C393083
91 Molex connector	4			LCSC	C293362
92 PWM Fan Header 1x4 (Standard)	2	PWM Fan Header 1x4 (Standard)		adafruit	
93 220nF		CL10B224KA8NNNC		LCSC	C21120
94 PNP Transistor	2	2N3906S-RTK/PS		LCSC	C147294
95 Current sensor		INA260AIPW	Texas Instruments		C181331
96 10uH		SCDS125T-100M-N		LCSC	C329747
97 5.6K		AR03BTC5601		LCSC	C309088
98 Inverter Gate Array		SN74LVC3G04DCUR	Texas Instruments		C153799
99 5.1K		AR03DTDX5101		LCSC	C319560
100 Connector		MTP125-1102S1		LCSC	C358684
101 NAND Gate		SN74ACT00DR	Texas Instruments		C352946
102 OPAMP		ADA4700-1	Analog Devices		C207958